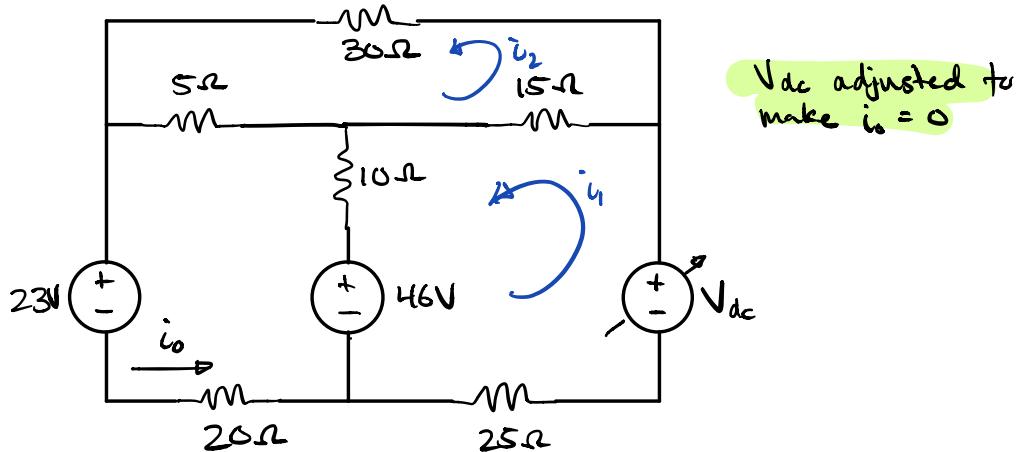


ENGR 221, HW#5, Due 5/31/20, Sean Lai

CH 4: #'s 58, 62, 72ab*, 74, 78, 82, 93
 * LTSpice. see assignment desc.

4.58:

Given:



- Find:
- Would you use NVA or NCA? Explain.
 - Find V_{dc} using method from a)
 - Show $P_{dev} = P_{diss}$

Solution:

a) Use **NCA** since we know $i_0 = 0$, leaving 2 meshes to analyze.

b) 0: $+23V + 0(20) - 46V + 10(i_0 - i_1) + 5(i_0 - i_2) = 0$

1: $-V_{dc} + 15(i_1 - i_2) + 10(i_1 - i_0) + 46V + 25(i_1) = 0$

2: $30i_2 + 5(i_2 - i_0) + 15(i_2 - i_1) = 0$

i_1	i_2	V_{dc}	
-10	-5	0	23
$(15+10+25)(-15)$		-1	-46
(-15)	$(30+5+15)$	0	0

$\rightarrow V_{dc} = -45V$

$$\left. \begin{array}{l} i_1 = -2A \\ i_2 = -0.6A \\ V_{dc} = -45V \end{array} \right\}$$

→ continued


4.58 continued →

c) $P_{dev} = \overset{20}{22(i_0)} + -46(i_1) + V_{dc}(i_1)$, $V_{dc} = -45V$, $i = -2A$
 $P_{dev} = 182W$
 $P_{diss} = \overset{20}{i_0(20)} + i_1^2(10+25) + 15(|i_2 - i_1|^2) + i_2^2(30+5)$
 $P_{diss} = 182W$

→ $P_{dev} = P_{diss} = 182W$

4.62:




Given:

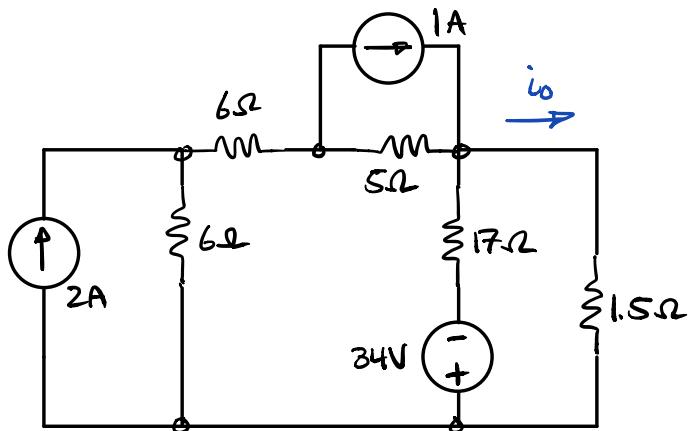

Find: a) Use source transforms to find i_o .
b) Verify by using NKA to find i_o .

Solution:


a) using $i_s = \frac{V_s}{R}$

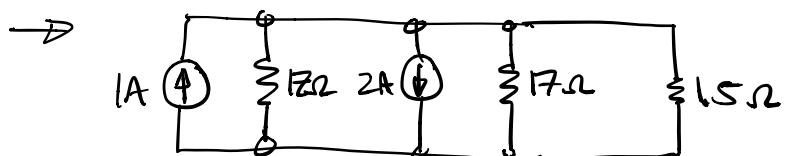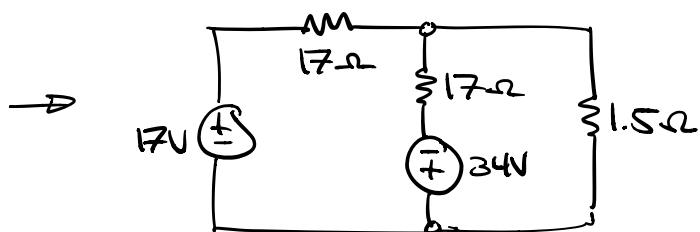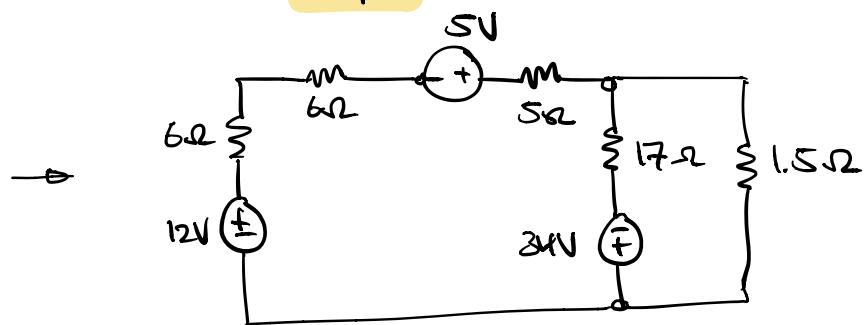

$\text{all in } \parallel \rightarrow I_{\text{eq}} = 1A \downarrow$
 $R_{\text{eq}} = 17 \parallel 17 = 8.5 \Omega$

continued →


4.62 continued

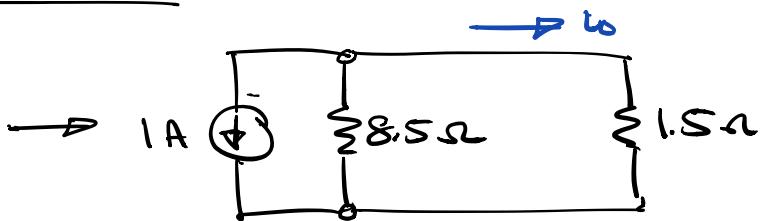

$$i_b = \frac{8.5}{10} = 1A$$

$$i_b = -0.85A$$

b)

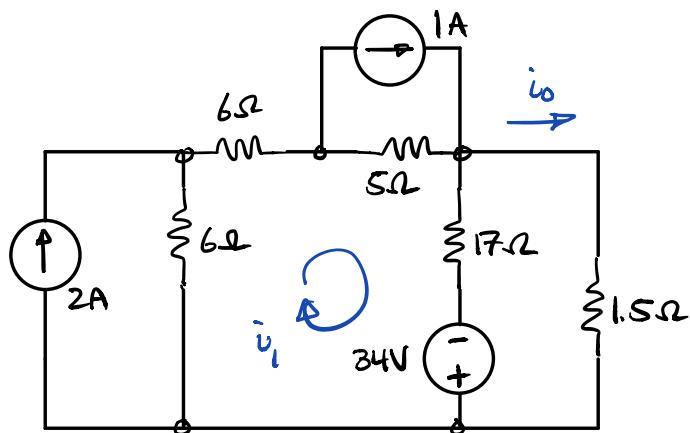

$$0: 1.5(i_o) + 34 + 17(i_o - i_1) = 0$$


$$1: 6(i_1 - 2) + 6(i_1) + 5(i_1 - 1) + 17(i_1 - i_o) - 34 = 0$$

$$\rightarrow \left| \begin{array}{cc|c} i_o & i_1 & \\ \hline (1.5+17) & -17 & -34 \\ -17 & (6+6+5+17) & 34+12+5 \end{array} \right| \quad \left. \begin{array}{l} i_b = -0.85 \\ i_1 = 1.575 \end{array} \right\}$$

$$\rightarrow i_b = -0.85A \quad \checkmark$$

4.72:

Given:

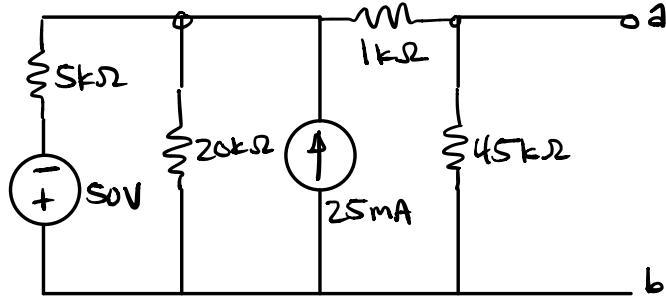

- Find:
- using LTspice, sim using ideal V meter, and one with 85.5kΩ resistance. Record findings
 - compare results using % error

Solution:

a) From LTSpice: 0Ω Vmeter : $V = 54V$


85.5Ω Vmeter: $V = 51.2849V$

b) $\% \text{Error} = \frac{-51.2849 - 54}{54} \cdot 100$
 $= -0.05 \cdot 100$

$\boxed{\% \text{Error} = -5\%}$

4.74:

Given:

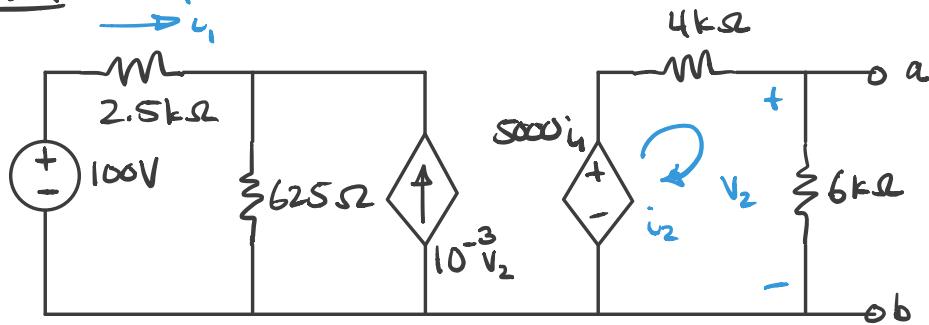

Find: Thévenin equivalent with respect to a, b

Solution:

$$OC: -100 + 2.5k(i_1) + 625(i_1 + 10^{-3}v_2) = 0$$

$$v_2 = \frac{6k}{4k+6k} \cdot 5000 i_1$$

i_1	v_2	0	$\left. \right\}$
$2500 + 625$	-10^{-3}		
$\frac{6}{10}(5000)$	-1	0	

$i_1 = 0.2A$
 $v_2 = 60V$

$$SC: v_2 = 0$$


$$i_{sc} = \frac{5000i_1}{4k}, \quad i_1 = \frac{100V}{2500 + 625}$$

$$i_1 = 0.032A$$

$$\Rightarrow i_{sc} = 0.04A$$


$$R_{TH} = \frac{v_{oc}}{i_{sc}} = \frac{60V}{0.04A}$$

$$R_{TH} = 1500\Omega$$

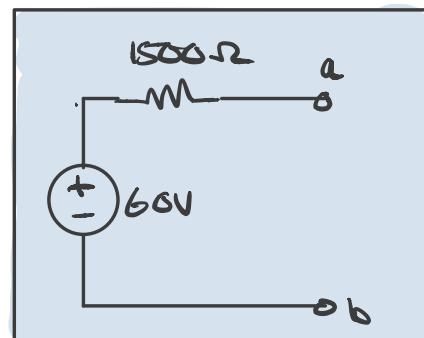

4.78:

Given:

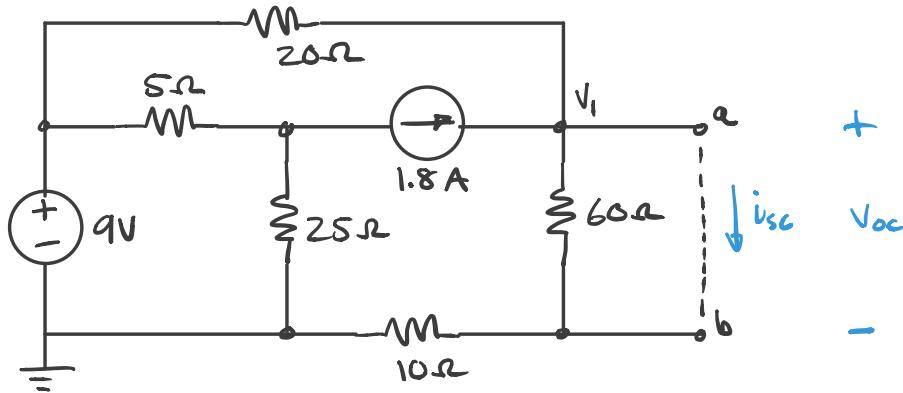

- Find:
- Thévenin equivalent w/ respect to a, b
 - Thévenin resistance with sources removed.
compare w/ a)

Solution:

$$DC: \frac{V_1 - 9}{20} + \frac{V_1}{70} - 1.8 = 0$$

$$\left(\frac{1}{20} + \frac{1}{70}\right)V_1 = 1.8 + \frac{9}{20}$$

$$V_1 = 35V$$

$$V_{OC} = V_1 \cdot \frac{60}{70}$$

$$\rightarrow V_{OC} = 30V$$

$$SC: \frac{V_1 - 9}{20} + \frac{V_1}{10} - 1.8 = 0$$

$$\left(\frac{1}{20} + \frac{1}{10}\right)V_1 = 1.8 + \frac{9}{20}$$

$$V_1 = 15V$$


$$i_{SC} = \frac{V_1}{10\Omega}$$

$$i_{SC} = 1.5A$$

$$\rightarrow R_{TH} = \frac{V_{OC}}{i_{SC}}$$

$R_{TH} = 20\Omega$
$V_{TH} = 30V$

CONTINUED

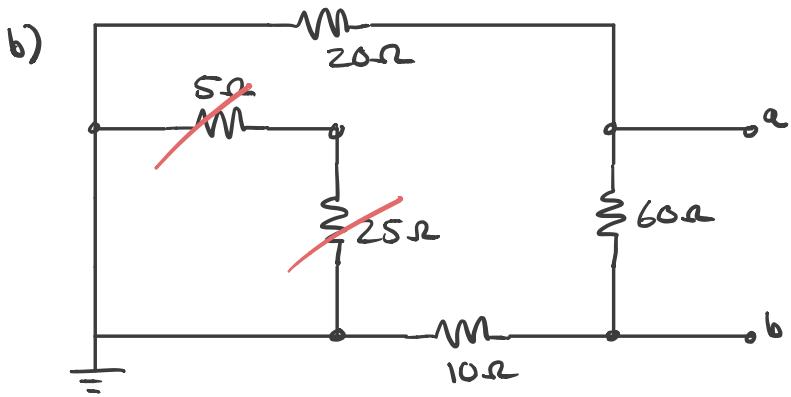

$$R_{ab} = 60 \parallel (20 + 10)$$


$$= 60 \parallel 30$$

$R_{ab} = 20\Omega$

✓

4.82:

Given:

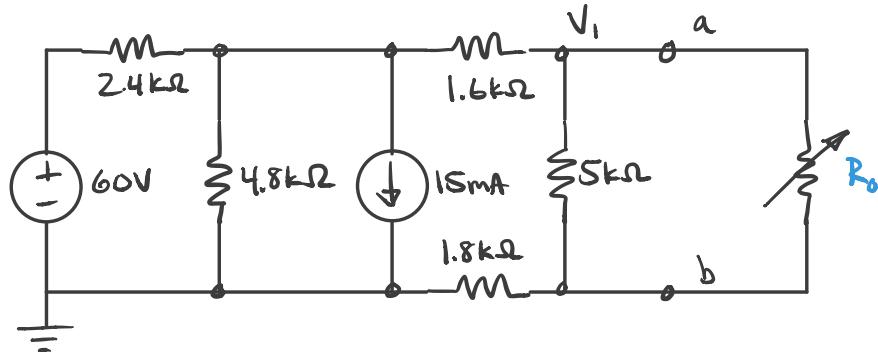


R_o adjusted for maximum power transfer

Find:

- R_o
- P_{max} delivered to R_o
- Resistor in Appendix H closest to R_o . How much power is delivered to that resistor?

Solution:

Find R_{TH} for a|b.

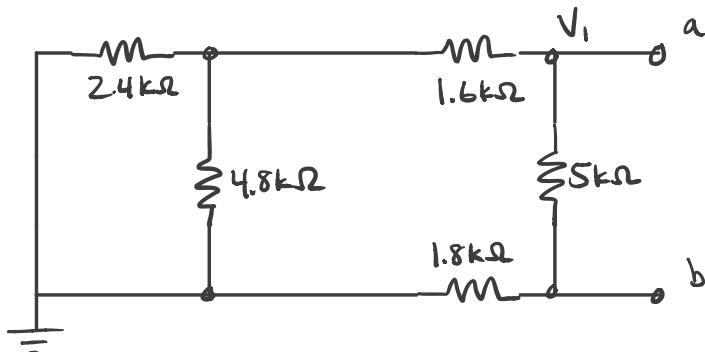

$$R_{TH} = 5000 \parallel (1600 + (2400 \parallel 4800) + 1800)$$


$$R_{TH} = 2500 \Omega$$

a) Max power when $R_o = R_{TH}$

$$\rightarrow R_o = 2500 \Omega$$

CONTINUED



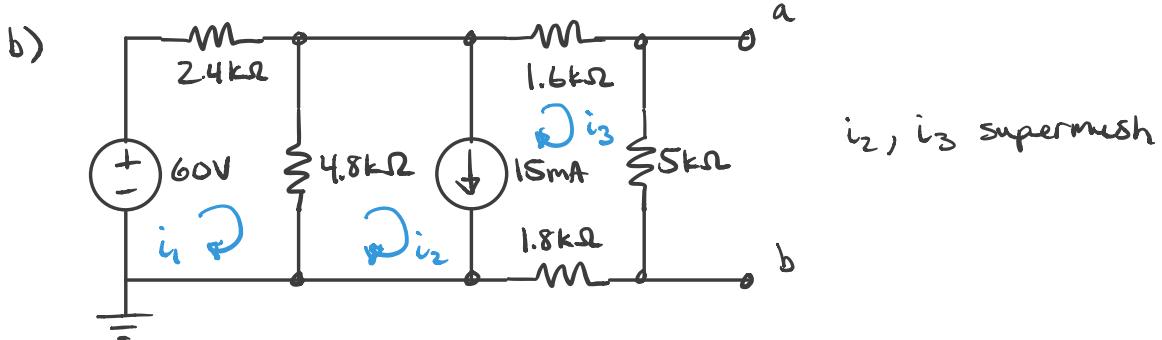

i_2, i_3 supermush

$$-60 + 2400(i_1) + 4800(i_1 - i_2) = 0$$


$$4800(i_2 - i_1) + 8400i_3 = 0$$

$$i_2 - i_3 = 0.015$$

i_1	i_2	i_3	
$2400 + 4800$	-4800		60
-4800	4800	8400	0
0	1	-1	0.015

$i_1 = 0.0194$
 $i_2 = 0.0166$
 $i_3 = 0.0016$

$$V_{oc} = i_3 \cdot 5k \\ = 8V$$

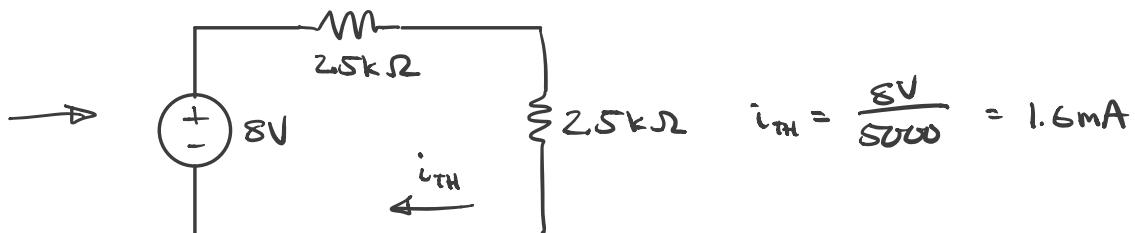

$$\rightarrow P_{max} = i_{TH}^2 (2500)$$

$$P_{max} = 6.4 \text{ mW}$$

c) $2.7k\Omega$ is closest.


$$i = \frac{8V}{5200} = 0.00154 \text{ A}$$

$$P_{max} = i^2 (2700)$$

$$P_{max} = 6.39 \text{ mW}$$

4.93:


Given:

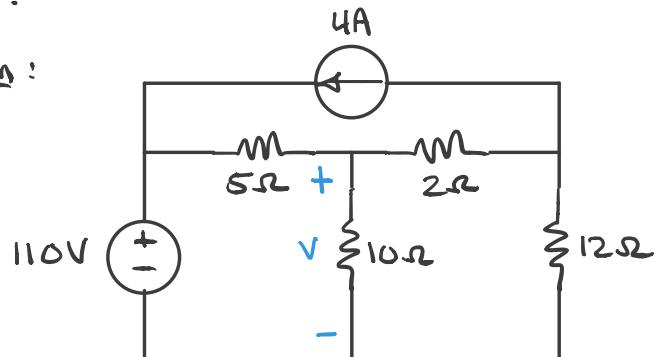

Find: a) Use superposition to find v
b) $P_{10\Omega}$

Solution:

a) Deactivate current source

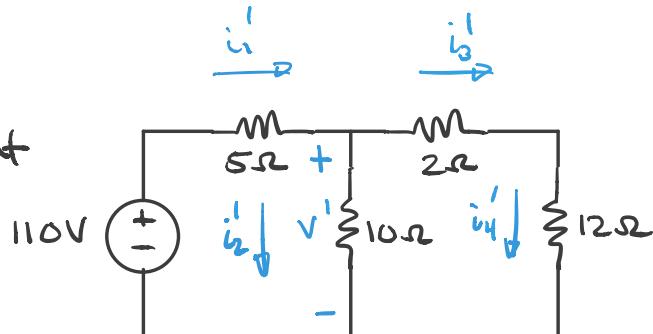

$$\rightarrow \frac{v' - 110}{5} + \frac{v'}{10} + \frac{v'}{14} = 0$$

$$v' \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{14} \right) = \frac{110}{5}$$

$$v' = 59.23 V$$


$$i_1' = \frac{110 - 59.23}{5} = 10.154 A$$

$$i_2' = \frac{59.23}{10} = 5.923 A$$

$$i_3' = i_4' = \frac{59.23}{14} = 4.231 A$$

CONTINUED
→

Deactivate Voltage Source:

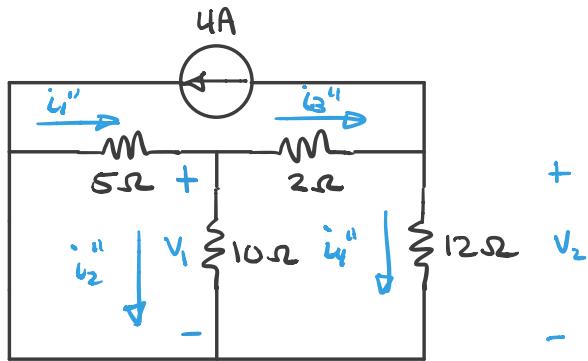

$$\frac{V_1}{5} + \frac{V_1}{10} + \frac{V_1 - V_2}{2} = 0$$

$$\frac{V_2}{12} + \frac{V_2 - V_1}{2} + 4 = 0$$

$$\begin{aligned} V_1 \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{2} \right) + V_2 \left(-\frac{1}{2} \right) &= 0 \\ V_1 \left(-\frac{1}{2} \right) + V_2 \left(\frac{1}{12} + \frac{1}{2} \right) &= -4 \\ V_2 &= 1.6 V_1 \end{aligned}$$

$$V_1 \left(-\frac{1}{2} + 1.6 \left(\frac{1}{12} + \frac{1}{2} \right) \right) = -4$$

$$V_1 = -9.23 \text{ V}$$

$$\rightarrow V = V' + V_1 \\ = 59.23' + -9.23$$

$$V = 50 \text{ V}$$

$$b) P_{10\Omega} = \frac{V^2}{R}$$

$$P_{10\Omega} = 250 \text{ W}$$