

## Homework 2, Problem 3

Sean Lai

October 11, 2019

Below is an image of the breadboard for the circuit specified in problem 3, showing also a resistance reading of  $209.2\Omega$  on the multimeter.

