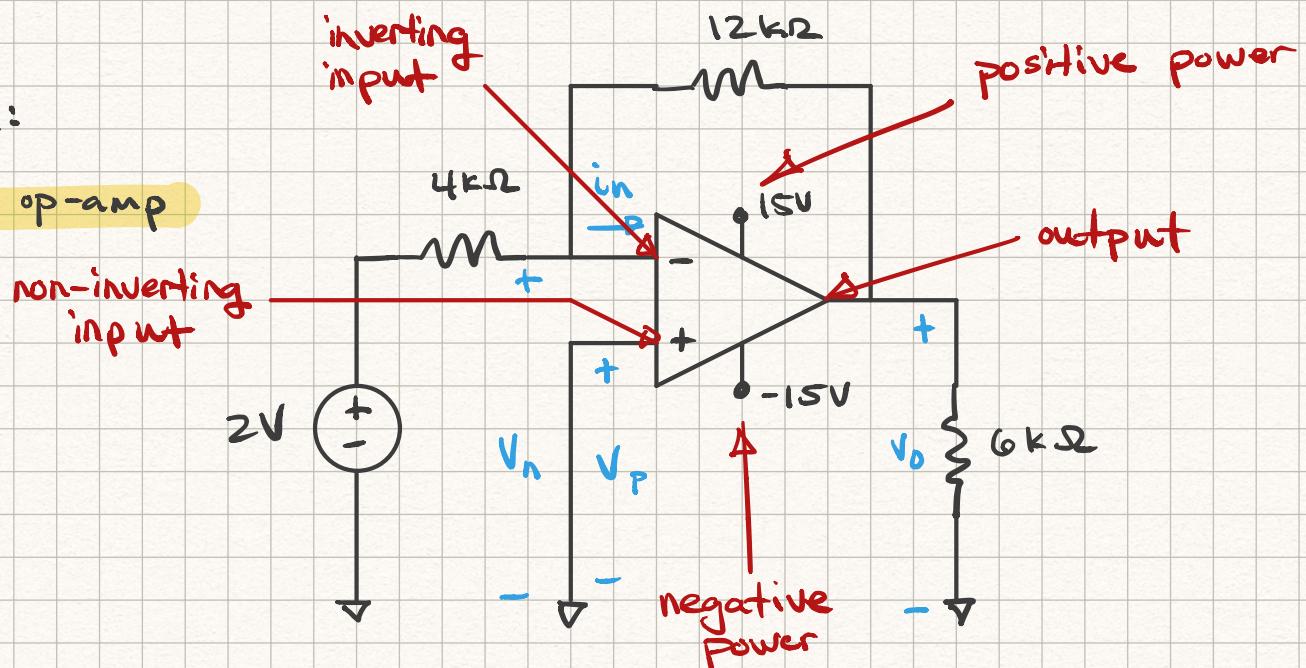


CH 5: 1, 6, 14, 15, 42, 48

S.1:Given:Find: a) Label 5 op-amp terminalsb) what op amp constraint determines i_{in} ? what value?c) " " " " " $V_p - V_n$? what value?d) Calculate V_o Solution:

a) See diagram

b) High input impedance, $i_{in} = 0$ c) Virtual short, $V_p - V_n = 0$

d) inverting amplifier

$$\rightarrow V_o = -V_n \left(\frac{R_f}{R_i} \right), \quad R_f = 12\text{k}\Omega, \quad R_i = 4\text{k}\Omega$$


$$\therefore V_o = 6V$$

S.6:

Given:

Ideal opamp :

15V rails

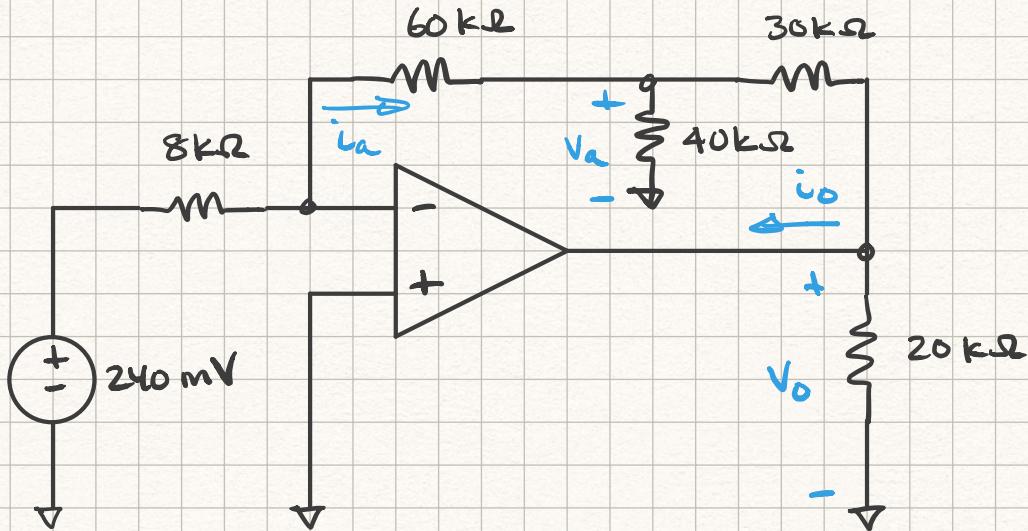

- Find:
- i_a
 - V_a
 - V_o
 - i_o

Solution:

a) $i_n = 0 \rightarrow i_a = \frac{0.240}{8000} = 3 \cdot 10^{-5} \text{ A}$

$\therefore i_a = 30 \mu\text{A}$

b) $V_n = V_p = 0 \rightarrow V_a - 0 = -i_a(60k)$

$V_a = -1.8 \text{ V}$

c) $\frac{V_a - V_o}{30k} = i_a - \frac{V_a}{40k}$


$V_o = -30k \left(i_a - \frac{V_a}{40k} \right) + V_a$

$V_o = -4.05 \text{ V}$

CONTINUED

5.6 CONTINUED

a)

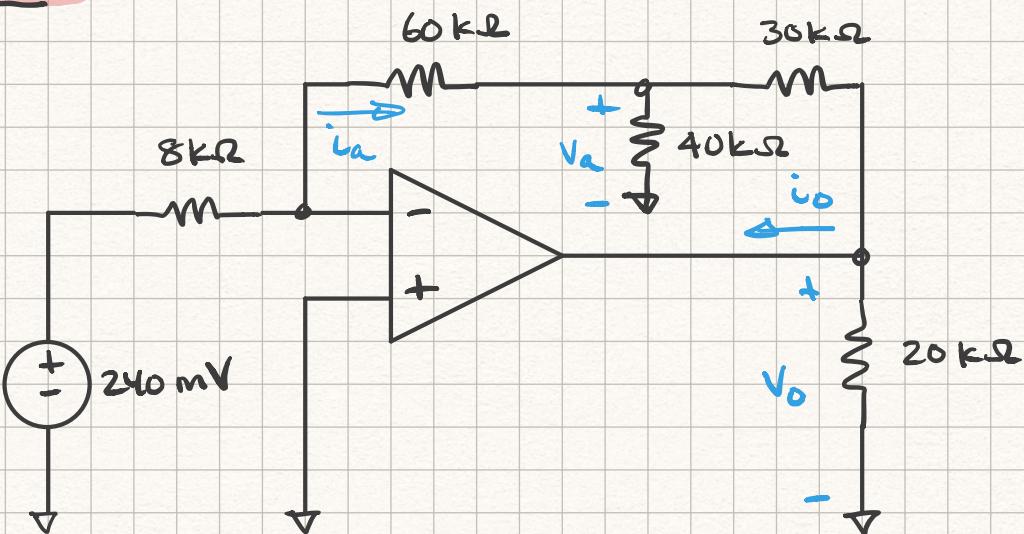

$$i_o + \frac{V_o}{20\text{k}} + \frac{V_o - V_a}{30\text{k}} = 0$$

$$i_o = -\frac{-4.05}{20\text{k}} - \frac{-4.05 - 1.8}{30\text{k}}$$

$$i_o = 2.775 \cdot 10^{-4} \text{ A}$$


$i_o = 277.5 \mu\text{A}$

5.14:

Given:

ideal op amp

+10V rails

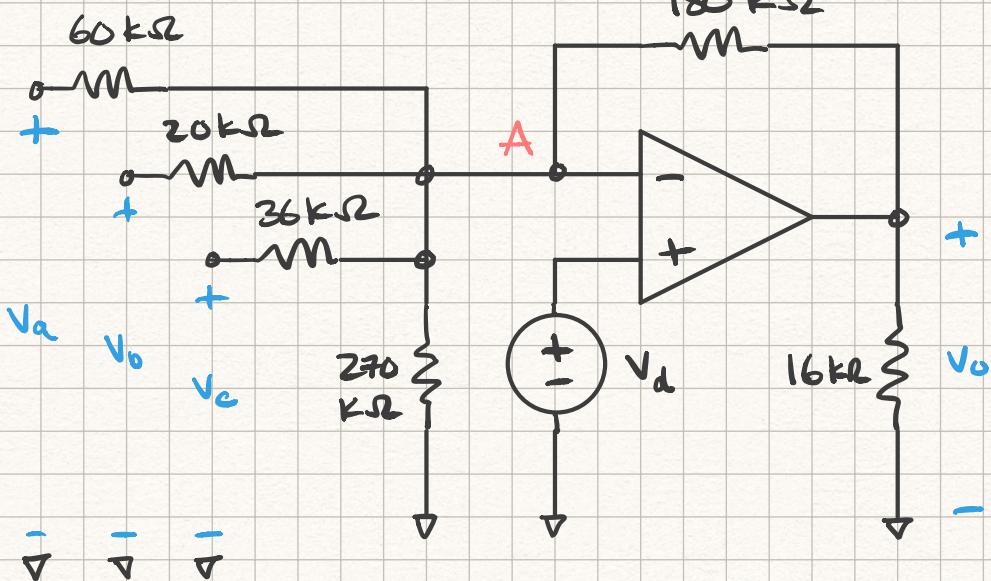

Find: a) Find V_o for $V_a = 3V$, $V_b = 9V$, $V_c = 5V$, $V_d = 6V$
 b) For $V_d = 6V$, specify range for V_c for linear region
 (no saturation)

Solution:

a) At A, $V = V_d$.

$$\rightarrow \frac{V_d - V_a}{60k} + \frac{V_d - V_b}{20k} + \frac{V_d - V_c}{36k} + \frac{V_d}{270k} + \frac{V_d - V_o}{180k} = 0$$

$$\rightarrow V_o = 180k \left[\frac{V_d - V_a}{60k} + \frac{V_d - V_b}{20k} + \frac{V_d - V_c}{36k} + \frac{V_d}{270k} + \frac{V_d}{180k} \right]$$

$$V_o = -3V$$

$$b) V_o = 180k \left[\frac{V_d - V_a}{60k} + \frac{V_d - V_b}{20k} + \frac{V_d - V_c}{36k} + \frac{V_d}{270k} + \frac{V_d}{180k} \right]$$

$$V_o = 180k \left[\frac{V_d - V_a}{60k} + \frac{V_d - V_b}{20k} + \frac{V_d}{36k} + \frac{V_d}{270k} + \frac{V_d}{180k} \right] - 5V_c$$

$$V_o = 22V - 5V_c$$

$$\text{For } V_o = +10V \rightarrow V_c = 2.4V$$


$$V_o = -10V \rightarrow V_c = 6.4V$$

$$2.4V \leq V_c \leq 6.4V$$

S.15:

Given:

ideal op amp
 $\pm 10V$ rails

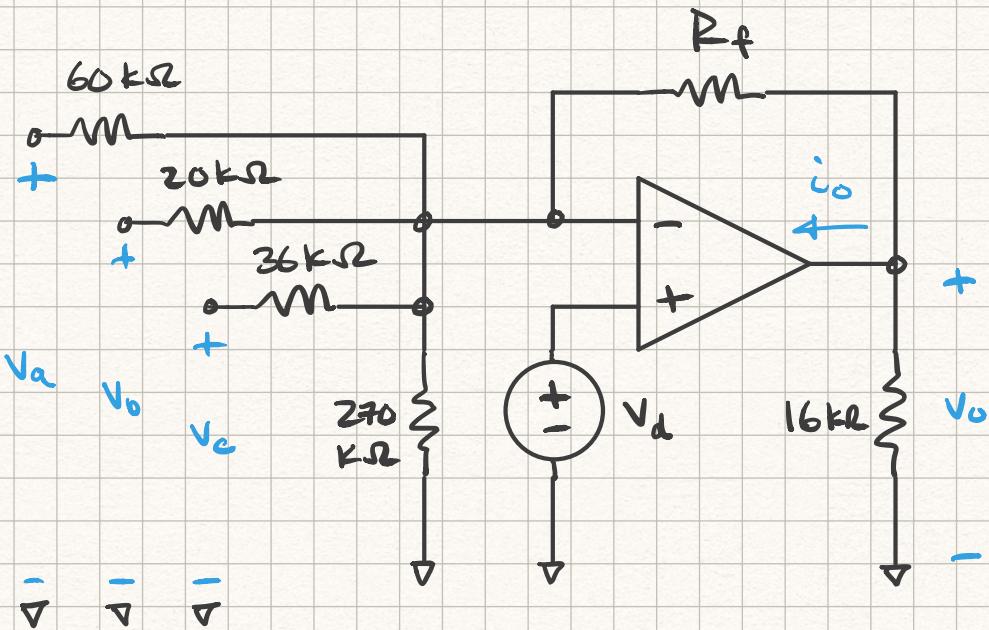

$$V_a = 3V, V_b = 9V, V_c = 5V, V_d = 6V$$

- Find: a) What R_f will cause saturation
 b) With R_f value from a), find i_o (μA)

Solution:

$$\frac{V_d - V_a}{60k} + \frac{V_d - V_b}{20k} + \frac{V_d - V_c}{36k} + \frac{V_d}{270k} + \frac{V_d - V_o}{R_f} = 0$$

$$R_f \left[\frac{V_d - V_a}{60k} + \frac{V_d - V_b}{20k} + \frac{V_d - V_c}{36k} + \frac{V_d}{270k} \right] + V_d = V_o$$

$-50\mu A$

for $V_o = +10V$,

$$10V = 6V + R_f(-50\mu A)$$

$$R_f = -80k \rightarrow \text{neg. resistance} \quad \times$$

for $V_o = -10V$,

$$-10V = 6V + R_f(-50\mu A)$$

a)

$$\rightarrow R_f = 320k \Omega$$


$$b) \frac{V_o}{16k} + i_o + \frac{V_o - V_d}{R_f} = 0$$

$$\rightarrow i_o = 675 \mu A$$

S.42:

Given:

$\pm 20V$ rails

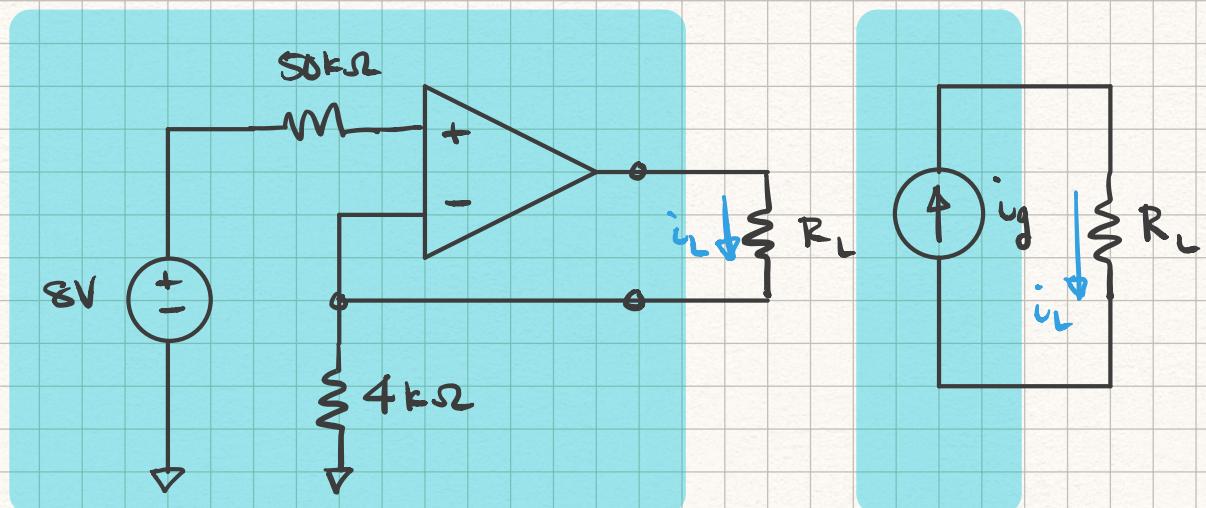

Find: a) Find i_L for $R_L = 4k\Omega$

b) Find max R_L for which i_L has value from a)

c) For $R_L = 16k\Omega$, $i_p = i_L \approx 0$, explain circuit operation

d) sketch i_L vs. R_L for $0 \leq R_L \leq 16k\Omega$

Solution:

a) for $i_p = 0$, $V_p = 8V = V_n$

$$\rightarrow \frac{V_n}{4000} + -i_L = 0$$

$$\therefore i_L = 2mA$$

b) For $V_o = \pm 20V$,

$$V_o = i_L (R_L + 4k\Omega)$$


$$R_L = \frac{V_o}{i_L} - 4k\Omega \quad , \text{ let } V_o = +20V$$

$$\therefore R_{L\max} = 6k\Omega$$

CONTINUED


5.42 CONTINUED

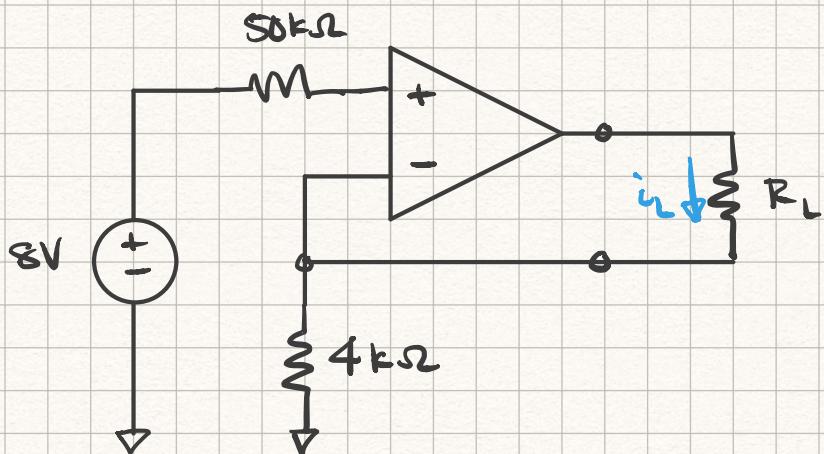c) $R_L = 16 \text{ k}\Omega$, $i_p = i_n \approx 0$



from b), for $R_L > 6 \text{ k}\Omega$, op amp is saturated, and
 $V_o = +20 \text{ V}$.

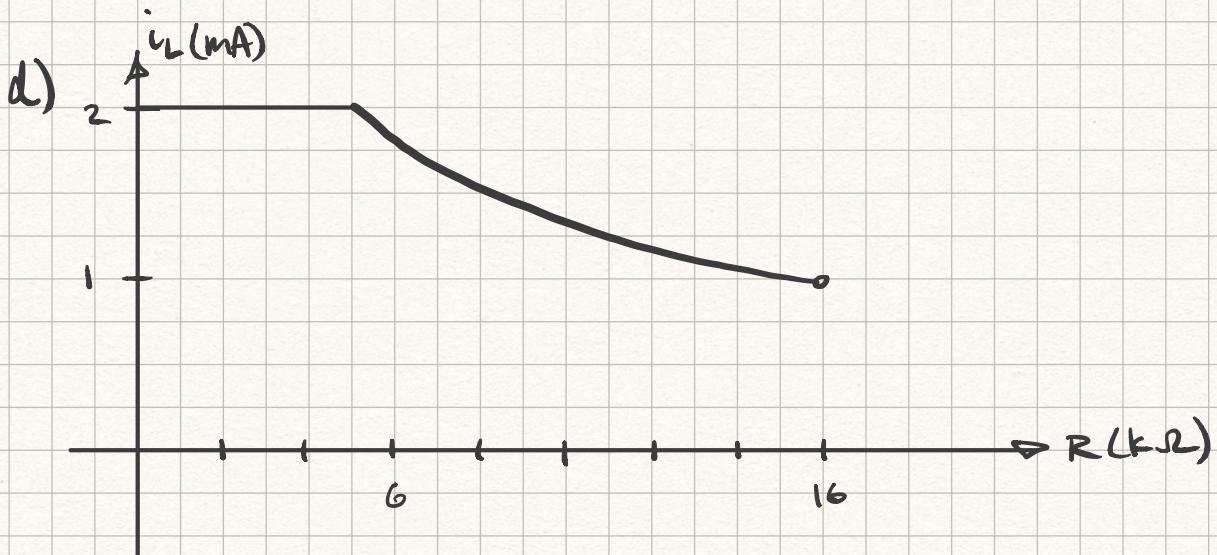So, for $R_L = 16 \text{ k}\Omega$, $i_L = \frac{20 \text{ V}}{16 \text{ k} + 4 \text{ k}} = 1 \text{ mA}$




$$i_L = \frac{V_o}{R_L + 4\text{k}} \quad \text{in saturation region}$$

$$\therefore i_L \propto \frac{1}{R_L}$$

5.48:

Given!

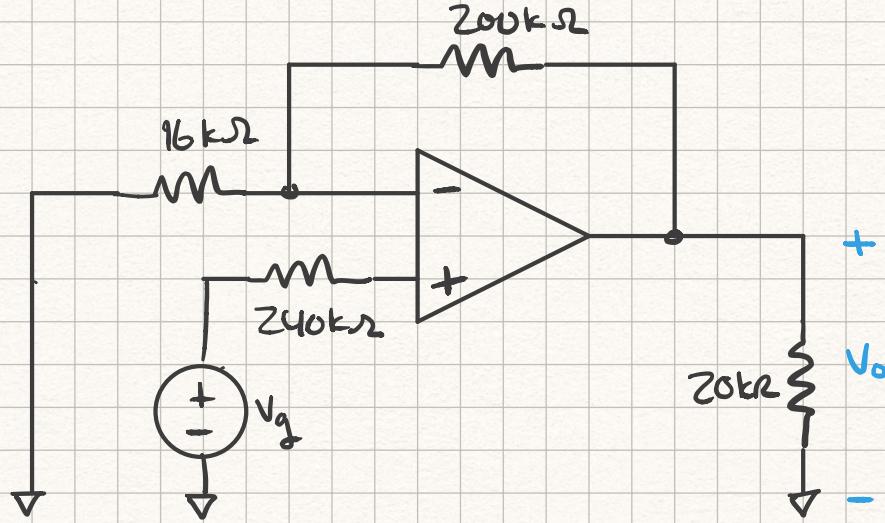

$\pm 15V$ rails
operating in linear region

Find: a) Voltage gain ($\frac{V_o}{V_g}$)


b) V_h , V_p in mV when $V_g = 1V$

c) $V_p - V_n$ in μV when $V_g = 1\text{V}$

d) current drain at V_g when $V_g = 1V$, in pA ($10^{-12} A$)

e) repeat a) - d) assuming ideal op amp

Solution:

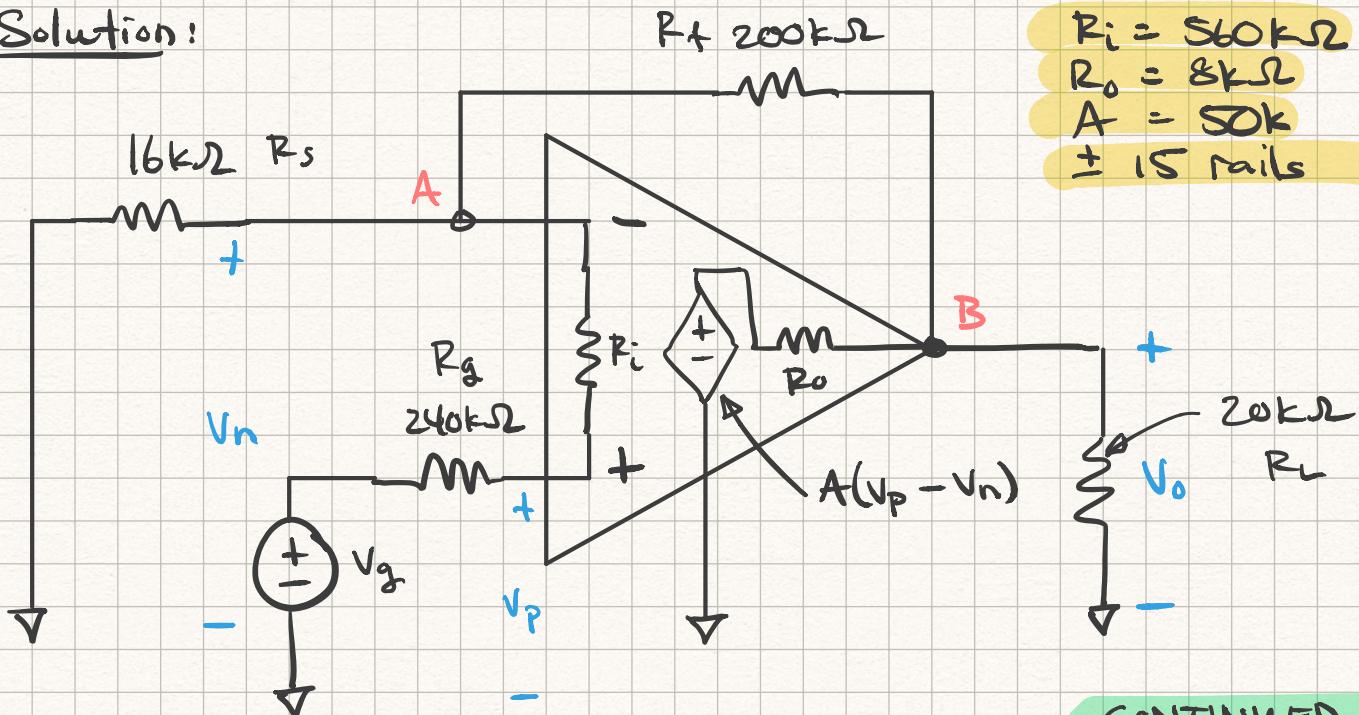

CONTINUED →

S.48 CONTINUED:

$$a) A: \frac{V_n}{R_s} + \frac{V_n - V_g}{R_g + R_i} + \frac{V_n - V_o}{R_f} = 0$$

$$B: \frac{V_o}{R_L} + \frac{V_o - V_n}{R_f} + \frac{V_o - A(V_p - V_n)}{R_o}$$

also, $V_p = \underbrace{(V_n - V_g) \left(\frac{R_g}{R_g + R_i} \right)}_{V \text{ divider}} + \underbrace{V_g}_{+ \text{offset}}$

into B:

$$V_o \left(\frac{1}{R_L} + \frac{1}{R_f} + \frac{1}{R_o} \right) + V_n \left(-\frac{1}{R_f} + \frac{A}{R_o} \right) - \frac{A}{R_o} \cdot \left[(V_n - V_g) \left(\frac{R_g}{R_g + R_i} \right) + V_g \right] = 0$$

$$\rightarrow c V_o + a V_n - \frac{A}{R_o} \cdot b V_n + \frac{A}{R_o} \cdot b V_g - \frac{A}{R_o} V_g = 0$$

$$V_o(c) + V_n(a - \frac{bA}{R_o}) + V_g \left(\frac{A}{R_o}(b-1) \right) = 0$$

where
 $a = 6.25$
 $b = 0.3$
 $c = 1.8 \cdot 10^{-4}$

$$\rightarrow V_o(c) + 4.375 V_n - 4.375 V_g = 0$$

$$V_n = V_g - \frac{c}{4.375} V_o$$

$$V_n = V_g - 4.114 \cdot 10^{-5} V_o$$

$$\text{into A: } \frac{V_n}{R_s} + \frac{V_n - V_g}{R_g + R_i} + \frac{V_n - V_o}{R_f} = 0$$

$$V_n \left(\frac{1}{R_s} + \frac{1}{R_g + R_i} + \frac{1}{R_f} \right) - V_g \left(\frac{1}{R_g + R_i} \right) - V_o \left(\frac{1}{R_f} \right) = 0$$

$$d = 6.875 \cdot 10^{-5}$$

CONTINUED

S.48 CONTINUED:

$$d(V_g - 4.114 \cdot 10^{-5} V_o) - 1.25 \cdot 10^{-6} V_g - 5 \cdot 10^{-6} V_o = 0$$

$$6.75 \cdot 10^{-5} V_g = 5 \cdot 10^{-6} V_o$$

$$\rightarrow \frac{V_o}{V_g} = 13.49$$

b) For $V_g = 1V$, $V_o = 13.49V$

$$\rightarrow V_n = 1V - 4.114 \cdot 10^{-5} (13.49V)$$

$$V_n = 999.445 \text{ mV}$$

$$V_p = (V_n - V_g) \left(\frac{R_g}{R_g + R_i} \right) + V_g$$

$$V_p = (999.445 - 1000)(0.3) + 1$$

$$V_p = 999.834 \text{ mV}$$

c)

$$V_p - V_n = 388.5 \mu V$$

$$d) i_g = \frac{V_g - V_p}{R_g}$$

$$i_g = 691.67 \text{ pA}$$