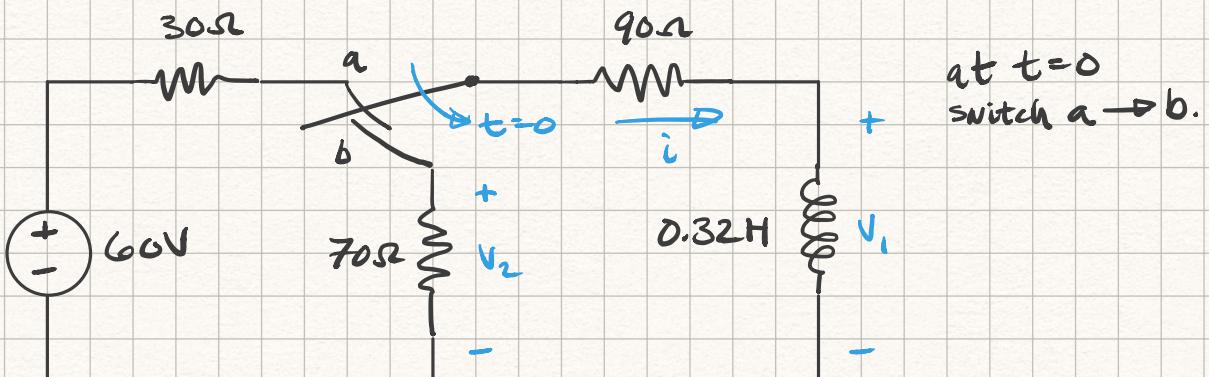


CH 7: 3, 52, 75

7.3:Given:

- Find:
- initial current in inductor  $i_0$
  - time constant  $\tau$  for  $t > 0$
  - $i$ ,  $V_1$ ,  $V_2$  for  $t \geq 0$
  - what % of initial energy in inductor is dissipated in  $90\Omega$  resistor at  $t = 1\text{ ms}$

Solution:

a) ind acts as s.c. in s.s.

$$\rightarrow i_0 = \frac{V}{R_{\text{eq}}}$$

$$i_0 = \frac{60V}{120\Omega}$$

∴

$$i_0 = 0.5A$$

$$\delta) R_{\text{thb}} = 160\Omega$$


$$\tau = \frac{L}{R_{\text{th}}}$$

$$\tau = \frac{0.32\text{ H}}{160\Omega}$$

∴

$$\tau = 2\text{ ms}$$

$$c) \text{ general eq: } X(t) = X_{ss} + (X_0 - X_{ss}) e^{-t/\tau}$$

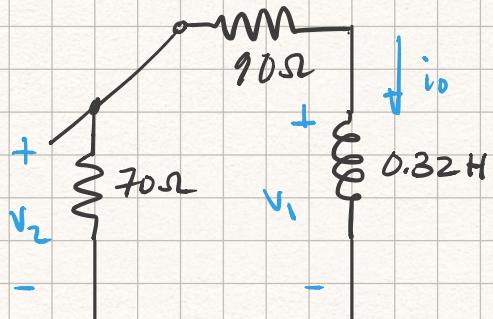
 $i_{ss} = 0$  as power will all dissipate

$$\therefore i(t) = i_0 e^{-t/\tau}$$

$$i(t) = 0.5 e^{-t/2\text{ ms}} \text{ A}$$

CONTINUED

### 7.3 continued:

$$V_1 : -i_0(90) - V_1 - i_0(70) = 0 \quad \text{initially}$$

$$\begin{aligned} V_{i_0} &= -i_0(90+70) \\ V_{i_0} &= -0.5(160) \\ V_{i_0} &= -80 \text{ V} \end{aligned}$$

$$V_{ss} = 0 \rightarrow V_1(t) = -80 e^{-t/2m} \text{ V}$$

$$V_2 : V_2 = -i(t)(70\Omega)$$

$$\rightarrow V_2(t) = -35 e^{-t/2m} \text{ V}$$

$$d) W_0 = \frac{1}{2} L i_0^2$$

$$W_0 = 0.04 \text{ J}$$

$$W_{q0}(t) = \int_0^t P dt, \quad P = i^2 R, \quad t_1 = 1 \text{ ns}$$

$$W_{q0}(t) = \int_0^t (0.5 e^{-t/2m})^2 \cdot 90 dt$$

$$W_{q0,1m} = 22.5 \int_0^{1m} e^{-t/1m} dt$$


$$\begin{aligned} W_{q0,1m} &= 22.5 \cdot 1m \left[ e^{-t/1m} \right] \Big|_0^{1m} \\ &= -22.5m [e^{-1} - 1] \end{aligned}$$

$$W_{q0,1m} = 0.01422 \text{ J}$$

$$\% \text{ diff} = \frac{0.01422}{0.04} \rightarrow \% \text{ loss} = 35.6 \%$$

7.52:

Given:

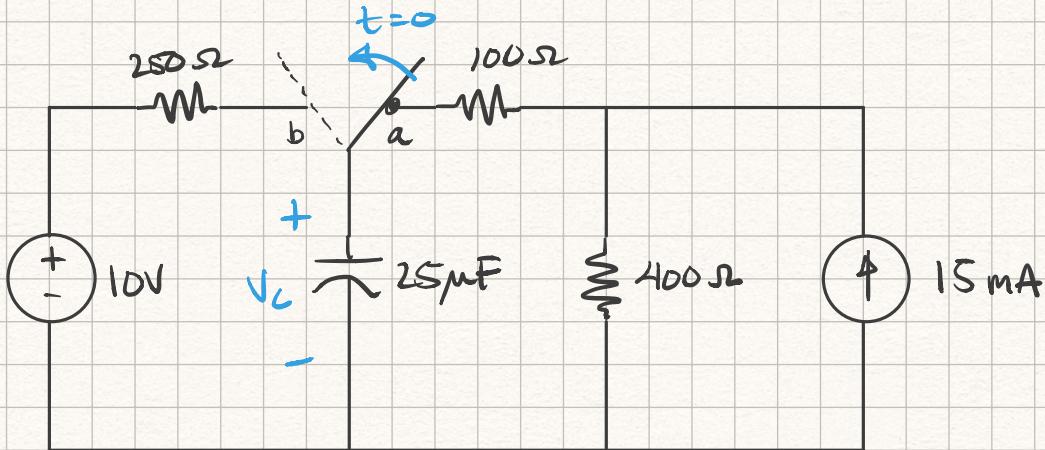

Find:

a)  $V_{CO}$ ,  $V_{CSS}$ ,  $\tau$  for  $t \geq 0$ , and  $v_c(t)$

b) assume pos. b for a long time and switched to a at  $t=0$ .  
find  $V_{CO}$ ,  $V_{CSS}$ ,  $\tau$ ,  $v_c(t)$

Solution:

a)  $R_{Tha} = 500\Omega$ ,  $i_{ca} = 0$

since  $i_{ca} = 0$ ,  $V_{400} = 15m \cdot 400$   
 $V_{400} = 6V$

$$\rightarrow V_{ca} - 0(100) = 6V = 0$$

$$V_{ca} = 6V$$

$$\rightarrow V_{CO} = 6V$$

at ss after switch to b,  $i_c = 0$

$$\rightarrow 10V - V_{CSS} = 0$$

$$\rightarrow V_{CSS} = 10V$$

$$R_{Thb} = 250\Omega$$

$$\tau = R_{Th} \cdot C \rightarrow \tau = 250 \cdot 25\mu$$

$$\tau = 6.25 \text{ ns}$$


$$v_c(t) = 10 + (6-10)e^{-\frac{t}{\tau}}$$

$$v_c(t) = 10 - 4e^{-\frac{t}{6.25}} \text{ V}$$

CONTINUED  
→

7.52 Continued:

b)

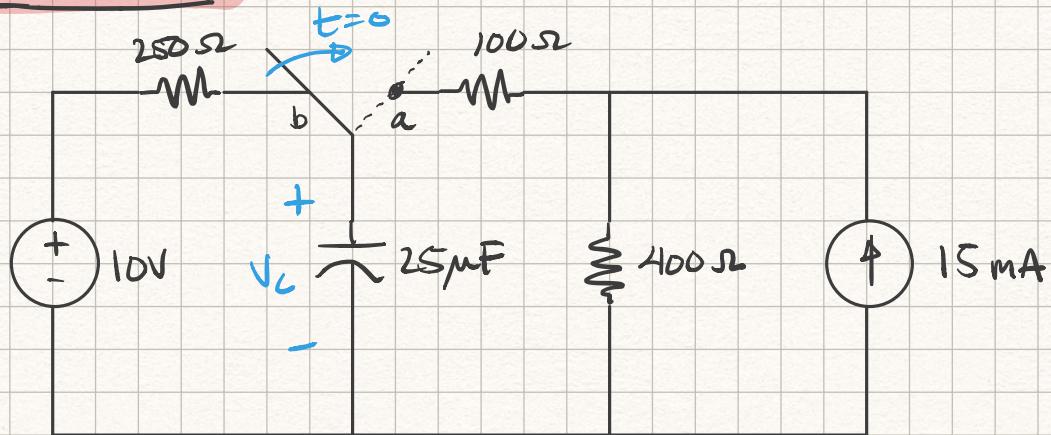

$$V_{CB} = 10V, V_{CSB} = 6V \leftarrow \text{solved in part a)}$$

$$R_{THA} = 500\Omega$$

$$\tau = 500 \cdot 25\mu$$

$$\tau = 12.5\text{ ms}$$



$$V_{CB} = 10V$$


$$V_{CSB} = 6V$$

$$\tau_b = 12.5\text{ ms}$$

$$V_{CB}(t) = 6 + 4e^{-80t} \text{ V}$$

7.75:

Given:

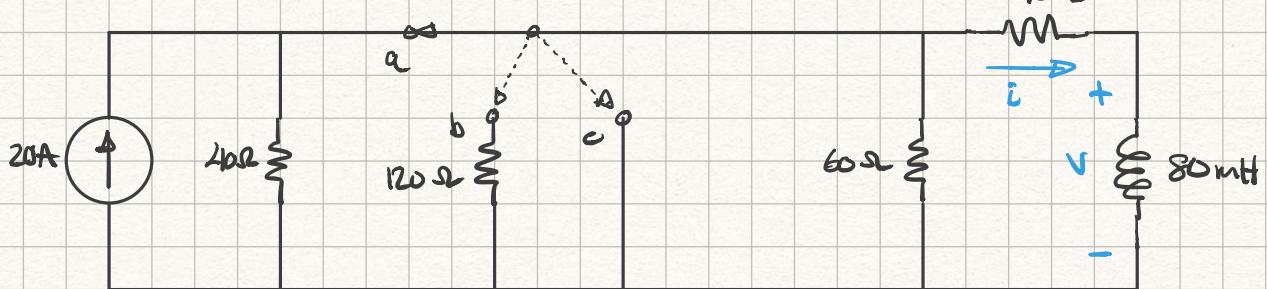

$$\begin{aligned} t < 0 &\rightarrow a \\ 0 \leq t < 1\text{ms} &\rightarrow b \\ t \geq 1\text{ms} &\rightarrow c \end{aligned}$$

Find:

- a)  $i(0^+)$
- b)  $i(200\mu\text{s})$
- c)  $i(6\text{ms})$
- d)  $V(1^- \text{ms})$
- e)  $V(1^+ \text{ms})$

Solution:

a) At s.s.,  $i = i_s \cdot \frac{60//40}{40 + 60//40}$

$$i(0^+) = 7.5\text{A}$$

b)  $i_{bs} = 0$

$$R_{thb} = 40 + 120//60 = 80\Omega$$

$$T_b = \frac{L}{R_{thb}} = 1\text{ms}$$

$$\rightarrow i_b(t) = 7.5e^{-1000t}$$

$$i_b(200\mu\text{s}) = 6.14\text{A}$$

c)  $i_{css} = 0$ ,  $i_o = i_b(1\text{ms}) = 2.76\text{A}$

$$R_{thc} = 40\Omega$$

$$T_c = 2\text{ms} \rightarrow i_c(t) = 2.76 e^{-500t}$$

$$i_c(6\text{ms}) = 226.5\text{mA}$$

note at  $t=6\text{ms}$ ,  
 $T_c = 5\text{ms}$

CONTINUED

$$d) v = L \frac{di}{dt}$$

$$v(1^-) = L \frac{\frac{di_b(t)}{dt}}{t=1^-}$$

$$v(1^-) = 80m \cdot -7500e^{-1000(1^-)}$$

$$v(1^-) = -220.73V$$

$$e) v(1^+m) = L \frac{\frac{di_b(t)}{dt}}{t_1=0m}$$

$$v(1^+m) = 80m \cdot -1380e^0$$

$$v(1^+m) = 110.4V$$