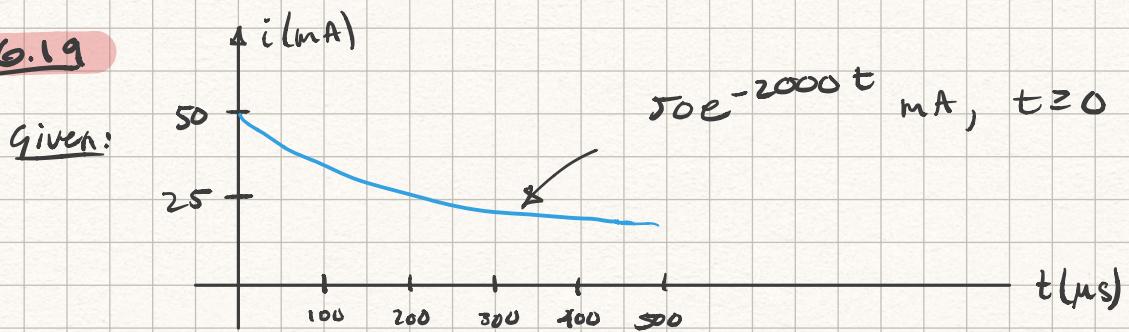


CH 6: 19, 23, 25, 28, 31, 39

6.19



Circuit diagram showing a capacitor  $C = 0.5 \mu F$  connected in series with a  $-20V$  DC voltage source. The current  $i$  flows through the circuit.

Find: a)  $E$  in  $\mu J$  is stored at  $t = 500 \mu s$   
 b) " " " " " " " "  $t = \infty$

2

Solution :

$$i = C \frac{dV}{dt} , \quad p = vi = CV \frac{dv}{dt} , \quad w = \frac{1}{2} CV^2$$

$$v(t) = \frac{1}{c} \int_0^t i d\tau + v(0) \quad , \quad v(0) = -20V$$

$$= \frac{1}{0.5e^{-6}} \int_0^{500e^{-6}} 50e^{-3} e^{-2e^3} dt - 20$$

$$= \frac{1}{0.5e^{-6}} \left[ \frac{50e^{-3}}{-2e^3} \left( e^{-2e^3 \cdot 500e^{-6}} - 1 \right) \right] - 20$$

$$= -5e^1 [e^{-1} - 1] - 20$$

$$V(\text{loops}) = 11.606 \text{ V}$$

$$W = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \cdot 0.5 \times 10^{-6} \cdot (11.606)^2$$

$$a) \quad w = 33,67 \mu J$$

$$b) v(\infty) = 30$$

$$W = \frac{1}{2} \cdot 0.5 \text{e-6} (20)^2 \rightarrow N = 225 \mu\text{J}$$

6.23:

Given: Using realistic inductor values in Appendix H. No energy stored

Find: Series /parallel combinations to yield equivalent inductances below. Minimize inductor count.

- a) 8 mH
- b) 45 μH
- c) 180 μH


Solution: inductors add like resistors.

Available inductors: 10 μH, 100 μH, 1 mH, 10 mH

$$a) L_{eq} = \left[ \frac{1}{L_1} + \frac{1}{L_2} + \dots \right]^{-1} + L_a + L_b + \dots$$

$$\frac{1}{8} = \frac{5}{40} = \left[ \frac{4}{40} + \frac{1}{40} \right]$$
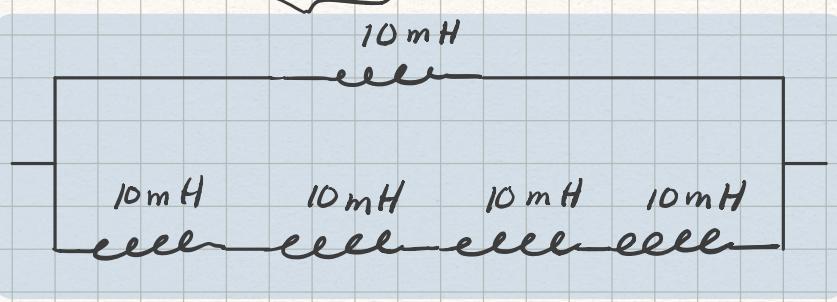
$$= \left[ \underbrace{\frac{1}{10} + \frac{1}{40}}_{10 \text{ mH}} \right]$$



$$b) 45 = 10 + 10 + 10 + 10 + 5 \quad 6 \text{ inductors...}$$

$$5 = 10 \parallel 10 \quad 2 \times L$$

$$40 \rightarrow \frac{1}{40} = \frac{5}{200} = \left[ \frac{2}{100} + \frac{1}{200} \right]$$

$$= 100 \parallel 100 \parallel 200 \quad 4 \times L$$

still 6

the simple one it is!




CONTINUED



6.23 Continued:

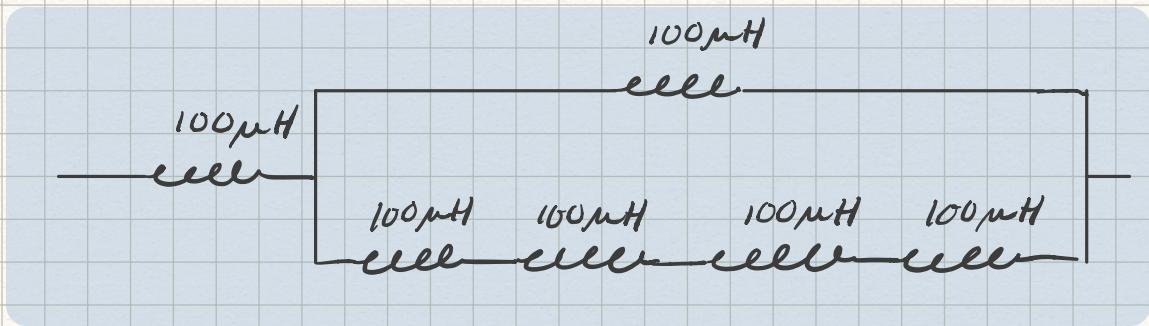
c)  $180 = 100 + \underbrace{80}_1$

$$\Leftrightarrow \frac{1}{80} = \frac{5}{400} = \left[ \underbrace{\frac{1}{100} + \frac{1}{400}}_5 \right]$$



6.25 :

Given:

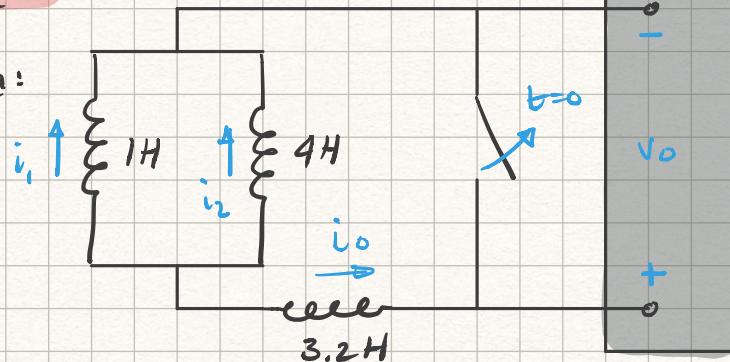

for  $t > 0$ :

$$V_0 = 2000 e^{-100t} \text{ V}$$

$$i_1(0) = -6 \text{ A}$$

$$i_2(0) = 1 \text{ A}$$

Find: a)  $i_0(0)$

b)  $i_0(t), t \geq 0$

c)  $i_1(t), t \geq 0$

d)  $i_2(t), t \geq 0$

e) initial energy stored in L's

f) total energy delivered to black box

g) energy trapped in the ideal L's

Solution:

$$\text{Leg} = 3.2 \text{ H} + 1//4$$

$$\text{Leg} = 4.0 \text{ H}$$

a)  $i_0(0) = -i_1 - i_2$   
 $= 6 \text{ A} - 1 \text{ A}$


$$i_0(0) = 5 \text{ A}$$

b)  $i_0(t) = \frac{1}{\text{Leg}} \int_0^t -2e^{3t} e^{-100t} dt + 5$

$$= -\frac{2000}{4 \cdot -100} [e^{-100t} - 1] + 5$$

$$i_0(t) = +5e^{-100t} \text{ A}$$

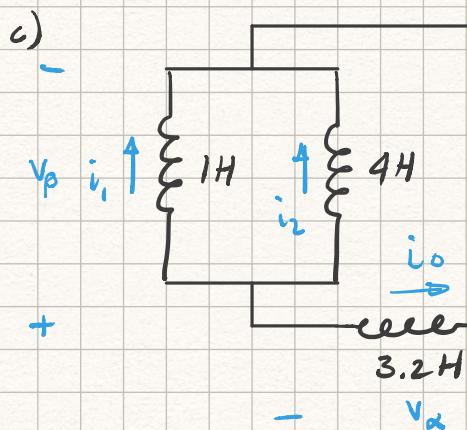note, voltage across Leg is neg. w/ respect to  $i_0$



CONTINUED

### 6.25 Continued :

$$V_0 = V_\alpha + V_\beta$$

$$V_\beta = V_0 - V_\alpha$$

now,  $V_\alpha = L \cdot -\frac{di_\alpha(t)}{dt}$

$$= 3.2H \cdot -5 \cdot -100e^{-100t}$$

$$= 1600 e^{-100t}$$

$$V_\beta = 2000e^{-100t} - 1600e^{-100t}$$

$$V_\beta = 400e^{-100t}$$

$$i_1(t) = \frac{1}{L_1} \int_0^t 400e^{-100\tau} d\tau + -6$$

$$i_1(t) = -4(e^{-100t} - 1) - 6$$

c)  $i_1(t) = -4e^{-100t} - 2A$

d)  $i_2(t) = \frac{1}{L_2} \int_0^t V_\beta d\tau + 1$

$$i_2(t) = -1(e^{-100t} - 1) + 1$$

$i_2(t) = -e^{-100t} + 2A$

e)  $N = \frac{1}{2} Li^2$

$$W = W_0 + W_1 + W_2$$

$$W = \frac{1}{2} [3.2(5)^2 + 1(6)^2 + 4(1)^2]$$

$W(0) = 60J$

f)  $W_{BB} = \frac{1}{2} L_{eq} i_{eq}^2$ ,  $L_{eq} = 4H$ ,  $i_{eq} = i_0(0) = 5A$

$$W_{BB} = \frac{1}{2} \cdot 4H \cdot 5A^2$$

$W_{BB} = 50J$

g)  $W_{trapped} = W(0) - W_{BB} \rightarrow W_{trapped} = 10J$

6.28:


Given: Using realistic caps in Appendix H

Find: Series / parallel combinations to yield capacitances below.  
Minimize capacitors.


- a)  $480 \mu F$
  - b)  $600 nF$
  - c)  $120 \mu F$

Solution :

$$a) \quad 10PF + 470PF$$

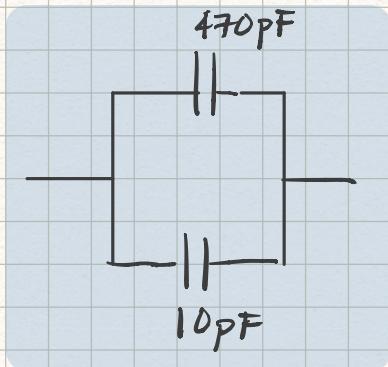

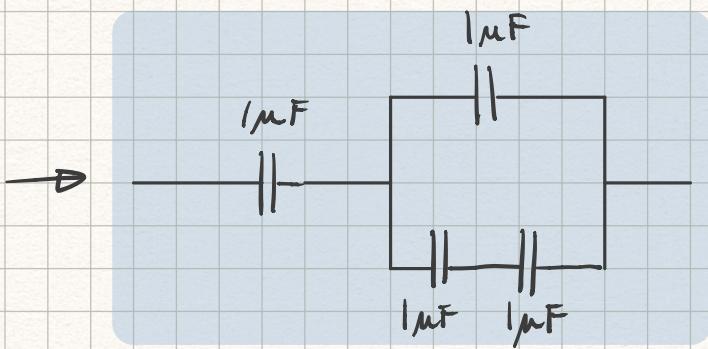
$$b) \frac{1}{600} = \frac{5}{3000} = \underbrace{\frac{1}{1000}}_{600\text{ nF}} + \underbrace{\frac{2}{3000}}_{1\mu F} = \frac{1}{1000} + \frac{1}{1500} = \frac{1}{1000} + \frac{1}{1000 + 500} = \frac{1}{1000} + \underbrace{\frac{1}{1000}}_{1m} + \underbrace{\frac{1}{500}}_{1\mu F + 1\mu m}$$



## CONTINUED


6.28 continued :

c)  $120\mu F = 100 + 10 + 10$

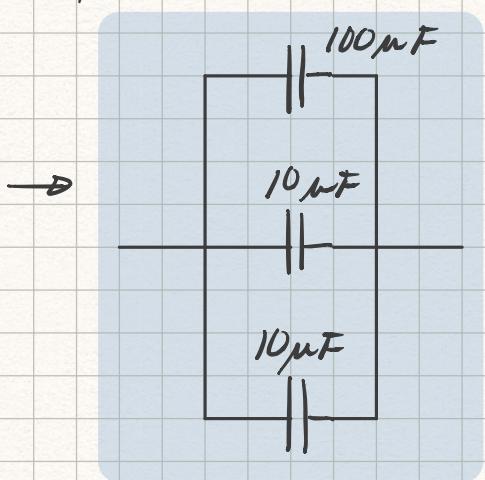

6.31:

Given:

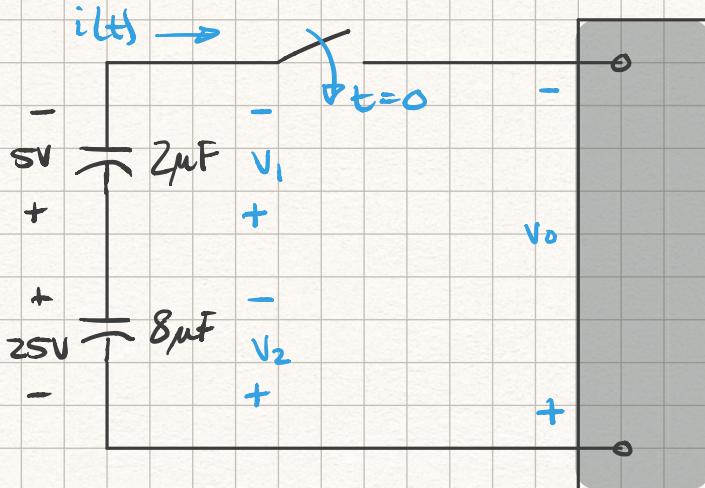

$$i(t) = 800e^{-25t} \mu A$$

- Find: a) use  $C_{eq}$  to find  $v_o(t)$  for  $t \geq 0$   
 b)  $v_1(t)$ ,  $t \geq 0$   
 c)  $v_2(t)$ ,  $t \geq 0$   
 d) energy delivered from  $0 \leq t < \infty$   
 e) energy initially stored in caps  
 f) energy trapped in ideal caps  
 g) show that  $v_1$  and  $v_2$  agree with part f)

Solution:

$$C_{eq} = C_1 \parallel C_2 \\ = \left( \frac{1}{2\mu} + \frac{1}{8\mu} \right)^{-1}$$

$$C_{eq} = 1.6 \mu F$$

$$v_o(t) = \frac{1}{C} \int_0^t i \, d\tau + v_o(0), \quad v_o(0) = -25 + 5 = -20V$$

$$v_o(t) = \frac{800e^{-6}}{1.6e^{-6}} \cdot -\frac{1}{25} \cdot \left[ e^{-25t} - 1 \right] - 20$$

$$v_o(t) = -20e^{-25t} + 20 - 20$$

a)  $v_o(t) = -20e^{-25t} V$

from figure,

b)  $v_1(t) = \frac{1}{C_1} \int_0^t i(\tau) d\tau + 5$

$$v_1(t) = \frac{800}{2} \cdot -\frac{1}{25} \left[ e^{-25t} - 1 \right] + 5$$

$v_1(t) = -16e^{-25t} + 21 V$

CONTINUED



6.31 Continued :

$$c) V_2(t) = \frac{1}{C_2} \int_0^t i(\tau) d\tau + -25$$

$$V_2(t) = \frac{800}{8} \cdot -\frac{1}{25} [e^{-25t} - 1] - 25$$

$$V_2(t) = -4e^{-25t} + 4 - 25$$

$$V_2(t) = -4e^{-25t} - 21 \text{ V}$$

$$d) W = \frac{1}{2} C V^2, \quad C = C_{eq}, \quad V = V_0(0) = -20$$

$$W = \frac{1}{2} (1.6 \mu F) (-20)^2$$

$$W_d = 320 \mu J$$

or check:

$$\begin{aligned} P &= -vi \\ P &= -(-20 e^{-25t})(800 \cdot 10^{-6} e^{-25t}) \\ P &= +1.6 \cdot 10^{-2} e^{-50t} \end{aligned}$$

$$dw = P dt$$

$$w = \int_0^\infty 1.6 \cdot 10^{-2} e^{-50t} dt$$

$$w = -3.2 \cdot 10^{-4} [0 - 1]$$

$$W_d = 320 \mu J \quad \checkmark$$

e)

$$\begin{aligned} w_i &= w_1 + w_2 \\ &= \frac{1}{2} [C_1 V_1(0)^2 + C_2 V_2(0)^2] \\ &= \frac{1}{2} [2\mu F (5)^2 + 8\mu F (-25)^2] \end{aligned}$$

$$w_i = 2525 \mu J$$

$$f) w_{\text{trapped}} = w_i - w_d$$

$$w_{\text{trapped}} = 2205 \mu J$$

CONTINUED



6.31 Continued:

$$g) v_1(t) = -16e^{-25t} + 21 \text{ V}$$

$$v_2(t) = -4e^{-25t} - 21 \text{ V}$$


as  $t \rightarrow \infty$ ,  $v_1(t) = 21 \text{ V}$   
 $v_2(t) = -21 \text{ V}$

$$\begin{aligned} W_{\text{trapped}} &= W_{1\infty} + W_{2\infty} \\ &= \frac{1}{2} [C_1(v_1)^2 + C_2(v_2)^2] \\ &= \frac{1}{2} (21)^2 [C_1 + C_2] \end{aligned}$$

$$W_{\text{trapped}} = 2205 \mu\text{J} \quad \checkmark$$

6.39:

Given:

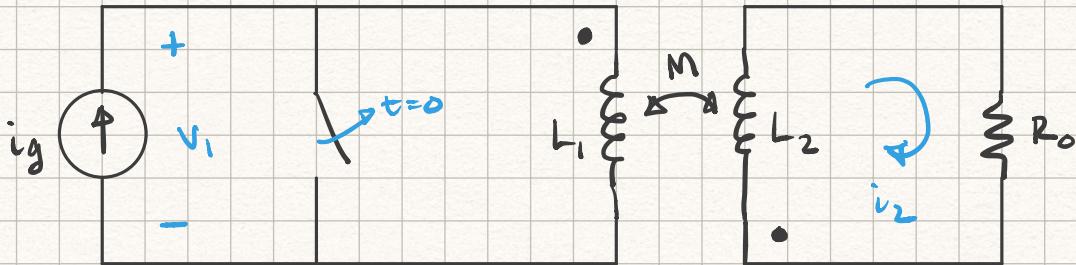

No initial energy stored

Find: a) Derive differential eq. for  $i_2$  if:

$$L_1 = 5H, L_2 = 0.2H$$

$$M = 0.5H, R_0 = 10\Omega$$


b) Show that for  $i_g = e^{-10t} - 10A, t \geq 0$ , eq. from a) is satisfied when  $i_2 = 625e^{-10t} - 250e^{-50t} \text{ mA}$

c) Find an expression for  $V_1$

d) What is the initial value of  $V_1$ ? Does this make sense in terms of known circuit behavior?

Solution:

a)

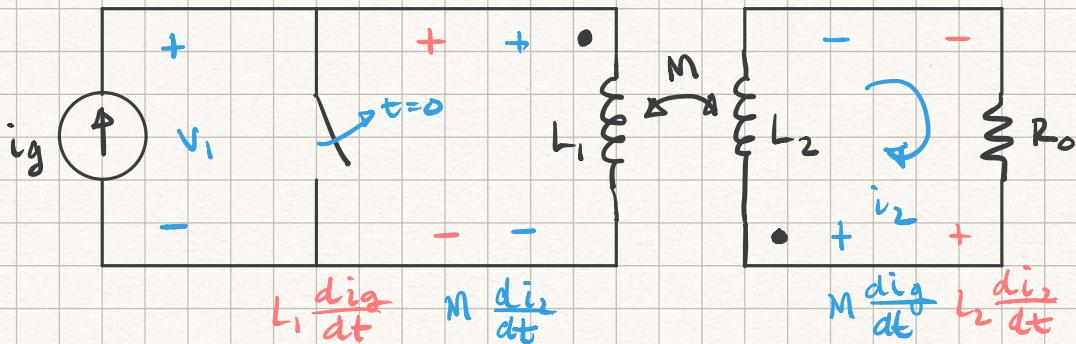

$$\text{mesh 1: } -V_1 + L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = 0$$

$$\text{mesh 2: } i_2 R_0 + L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = 0$$

$$\text{from mesh 2: } \frac{di_2}{dt} = \frac{1}{L_2} \left[ -i_2 R_0 - M \frac{di_1}{dt} \right]$$

$$\frac{di_2}{dt} = 5 \left[ -10i_2 - 0.5 \frac{di_1}{dt} \right]$$

$$\frac{di_2}{dt} = -50i_2 - 2.5 \frac{di_1}{dt}$$

CONTINUED

6.39 Continued:

b) let  $i_g = e^{-10t} - 10A$ ,  $i_2 = 625e^{-10t} - 250e^{-50t}$  mA

$$\frac{d}{dt}(i_2) = -50i_2 - 2.5 \frac{d}{dt}i_g$$

$$\frac{d}{dt}i_2 = -6.25e^{-10t} + 12.5e^{-50t} A$$

$$\frac{d}{dt}i_g = -10e^{-10t} A$$

$$\rightarrow -6.25e^{-10t} + 12.5e^{-50t} = -50(0.625e^{-10t} - 0.25e^{-50t}) \\ - 2.5(-10e^{-10t})$$

$$-6.25e^{-10t} + 12.5e^{-50t} = -31.25e^{-10t} + 25e^{-10t} + 12.5e^{-50t}$$

$$-6.25e^{-10t} + 12.5e^{-50t} = -6.25e^{-10t} + 12.5e^{-50t}$$

$$0 = 0 \quad \checkmark$$

c)  $V_1 = L_1 \frac{di_g}{dt} + M \frac{di_2}{dt}$

using values from b)

$$V_1 = 5(-10e^{-10t}) + 0.5(-6.25e^{-10t} + 12.5e^{-50t})$$

$$V_1 = -50e^{-10t} - 31.25e^{-10t} + 6.25e^{-50t}$$

$$V_1 = -53.125e^{-10t} + 6.25e^{-50t} V$$

d)  $V_1(0) = -46.875 V$  ← plugging  $t = 0$  into expression above.

The voltage should be negative when the switch is first flipped as  $L_1$  will induce a voltage against the source current  $i_g$ . Our calculated  $V_1$  is negative, so this makes sense.